

Huddle Board Exercise for Module 2 – No. 1
Monday, February 17, 2014

Draw the **AND-OR** realization and the **NAND-NAND** realization of the following function:

$$F(X,Y,Z) = X' \cdot Y \cdot Z + X \cdot Z' + Y' \cdot Z$$

Draw the **OR-AND** realization and the **NOR-NOR** realization of the following function:

$$F(X,Y,Z) = (X+Y'+Z) \cdot (X'+Y) \cdot (Y+Z')$$

Huddle Board Exercise for Module 2 – No. 1a
Monday, February 17, 2014

1. Assuming that *only true* variables are available, realize the function $F(X,Y,Z)$ mapped below three different ways:
- (a) Using only 7400 (quad 2-input NAND) chips
 - (b) Using only 7402 (quad 2-input NOR) chips
 - (c) Using only 7403 (quad 2-input open-drain NAND) chips

	X'		X	
Z'	1	d	0	1
Z	1	0	0	0
	Y'		Y	Y'

Show complete schematics for each realization, along with your derivations.

2. Equipped only with a bucket full of 2-input NAND gates (plus a breadboard, some wires, some SPST switches, an LED, some resistors, and a power supply), you must implement the function represented by the ON SET $\sum_{x,y,z}(0,1,7)$ as efficiently and quickly as possible. *Show all of your work, plus a complete schematic (including the switches, resistors, LED, and however many 2-input NAND gates deemed necessary).*

Huddle Board Exercise for Module 2 – No. 1b
Monday, February 17, 2014

Practice for standardized exam questions — determine the one best response.

The following K-map applies to questions 1 through 6:


		X'		X	
Z'	1	1	0	d	
Z	0	0	1	0	
	Y'		Y	Y'	

- Assuming the availability of **only true** input variables, the **fewest number of 2-input NAND gates** that are needed to realize this function is:
 (A) 6 (B) 7 (C) 8 (D) 9 (E) none of the above
- Assuming the availability of **only true** input variables, the **fewest number of 2-input NOR gates** that are needed to realize this function is:
 (A) 6 (B) 7 (C) 8 (D) 9 (E) none of the above
- Assuming the availability of **only true** input variables, the **fewest number of 2-input open-drain NAND gates** that are needed to realize this function is:
 (A) 6 (B) 7 (C) 8 (D) 9 (E) none of the above
- The **number of pull-up resistors** required for realizing this function as described in **question 3, above**, is:
 (A) 1 (B) 2 (C) 3 (D) 4 (E) none of the above
- The **cost of a minimal sum of products** realization of this function (assuming **both true and complemented variables** are available) would be:
 (A) 9 (B) 10 (C) 11 (D) 12 (E) none of the above
- The **cost of a minimal products of sum** realization of this function (assuming **both true and complemented variables** are available) would be:
 (A) 9 (B) 10 (C) 11 (D) 12 (E) none of the above

Huddle Board Exercise for Module 2 – No. 2

Wednesday, February 26, 2014

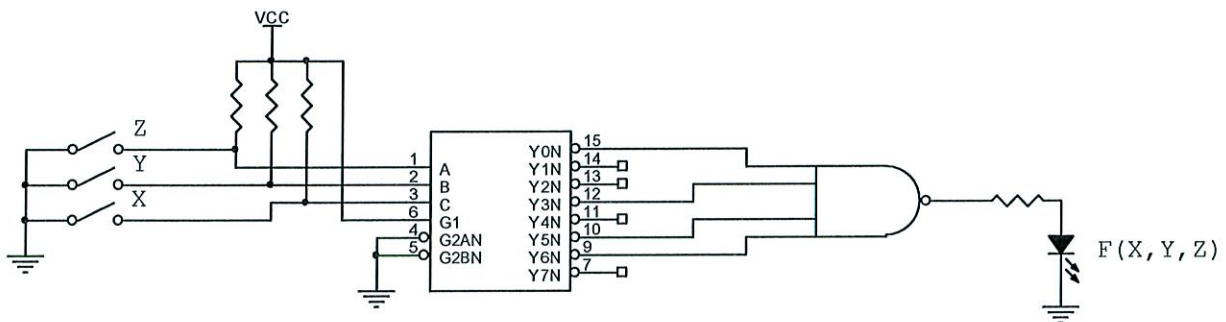Determine the **ON set** and a simplified **minimum sum-of-products** function realized by this decoder-based circuit.



Determine the **ON set** and a simplified **minimum sum-of-products** function realized by this decoder-based circuit.

