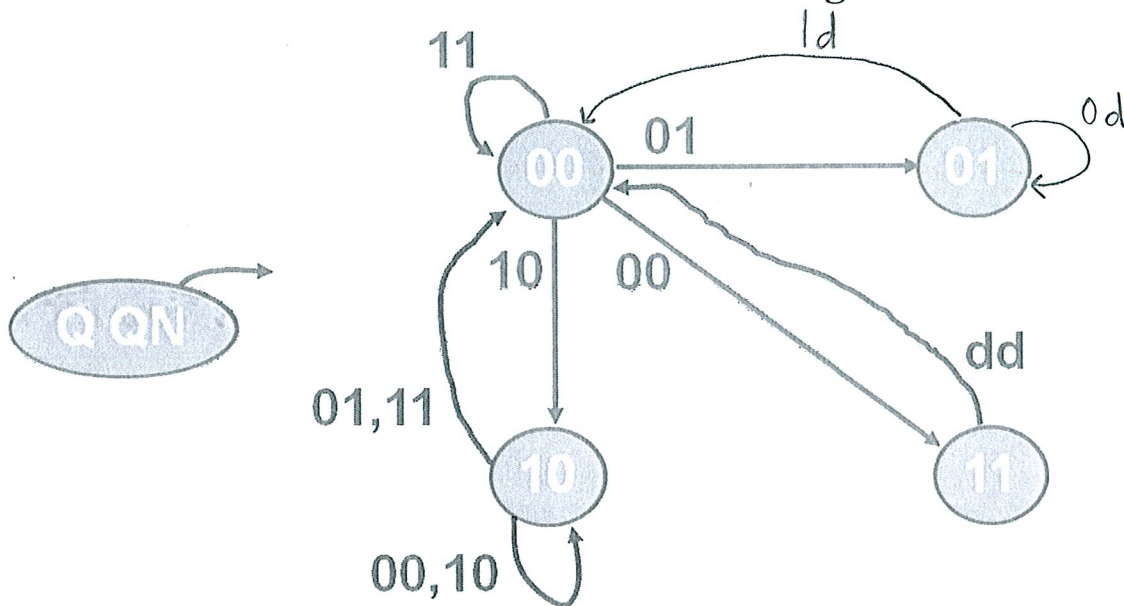


Huddle Board Exercise for Module 3 – No. 1
Monday, March 10, 2014

Use the following PS-NS table to construct a state transition diagram.


Present State Q(t) QN(t)	Present Inputs: S(t) R(t)			
	00	01	10	11
00	11	01	10	00
01	01	01	00	00
10	10	00	10	00
11	00	00	00	00

State Transition Diagram





Huddle Board Exercise for Module 3 – No. 2
Wednesday, March 12, 2014

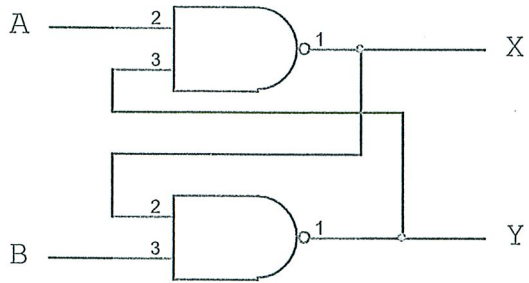Use the following **circuit** below to determine the **next state equations**, complete the **state transition diagram**, and complete the **present state – next state table**.



$$X(t+\tau) = \underline{A' + Y'}$$


$$Y(t+\tau) = \underline{B' + X'}$$

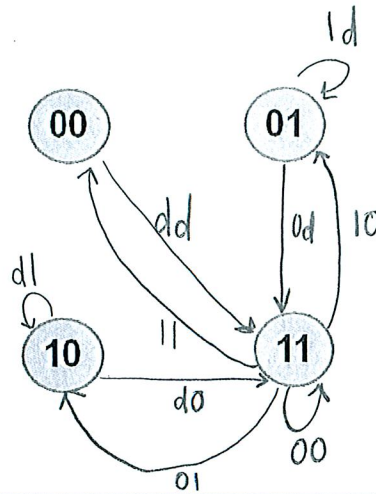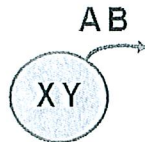


Present State	Present Input			
	A(t) B(t)			
X(t) Y(t)	0 0	0 1	1 0	1 1
0 0	1 1	1 1	1 1	1 1
0 1	1 1	1 1	0 1	0 1
1 0	1 1	1 0	1 1	1 0
1 1	1 1	1 0	0 1	0 0

Huddle Board Exercise for Module 3 – No. 3
Monday, March 24, 2014

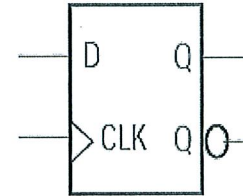Complete the timing chart for the edge-triggered flip-flop, below, assuming its $t_{PLH}(C \rightarrow Q)$ is 10 ns and its $t_{PHL}(C \rightarrow Q)$ is 5 ns.



→ | ← 5 ns

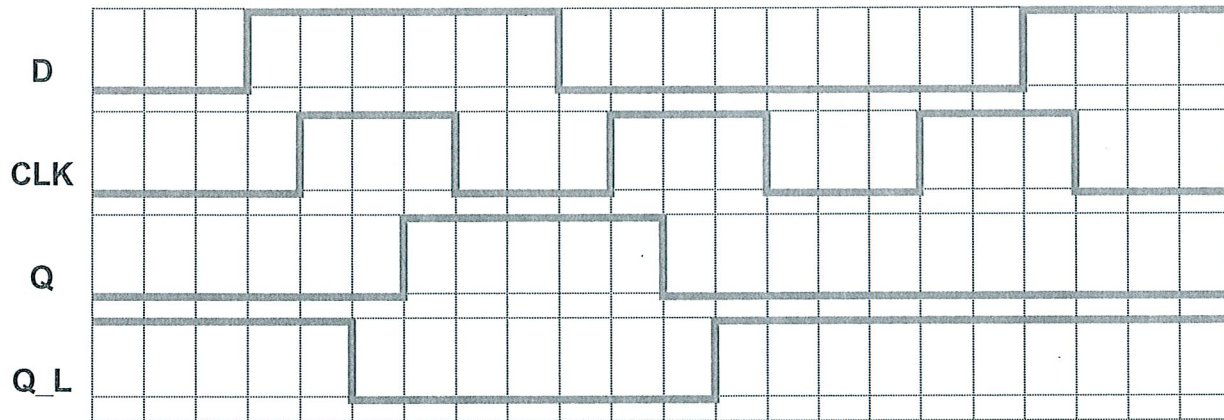

Determine the following:

- (a) the **nominal setup time** provided for the D flip-flop, based on the excitation signals (D and CLK) depicted in the timing chart: 5 ns

- (b) the **nominal hold time** provided for the D flip-flop, based on the excitation signals (D and CLK) depicted in the timing chart: 10 ns


- (c) the **nominal clock pulse width** provided for the D flip-flop, based on the excitation signals (D and CLK) depicted in the timing chart: 15 ns

- (d) the **duty cycle** of the clocking signal: 50%


Huddle Board Exercise for Module 3 – No. 4
Wednesday, March 26, 2014

Synthesize the state machine depicted by the following PS-NS table two different ways: using a D flip-flop and using a T flip-flop. Note that there are two inputs, A and B, along with a single state variable, X. Assume only *true* input variables are available, but you may use any types of gates deemed necessary. *Show all work.*

A	B	X	X*	D	T
0	0	0	1	1	1
0	0	1	1	1	0
0	1	0	1	1	1
0	1	1	1	1	0
1	0	0	0	0	0
1	0	1	0	0	1
1	1	0	1	1	1
1	1	1	0	0	1

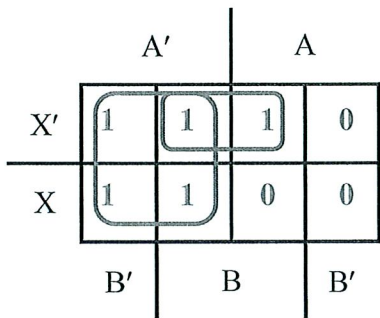



$$D = A' + X' \cdot B$$

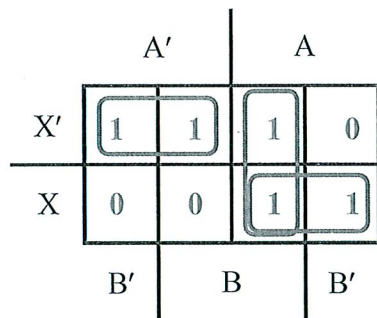

$$T = A' \cdot X' + A \cdot B + A \cdot X$$

D flip-flop implementation:


T flip-flop implementation:

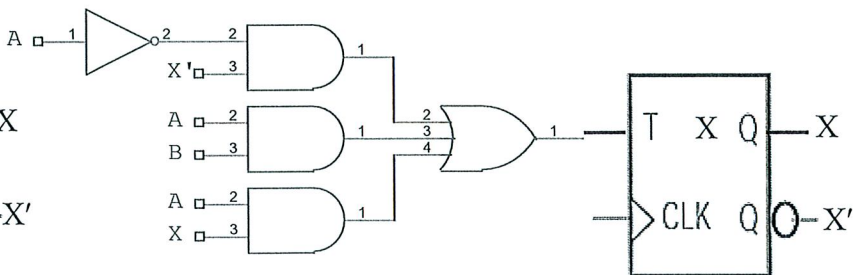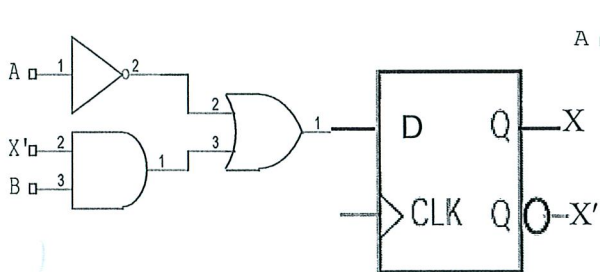


Huddle Board Exercise for Module 3 – No. 4a
Wednesday, March 26, 2014

Design a state machine that serves as a simple two-floor elevator controller. When the elevator is on floor one, the digit “1” should be output on a 7-segment display; when the elevator is on floor two, the digit “2” should be displayed. Input M should control the direction of the elevator: if M=0, the elevator should descend from floor two to floor one (and stay there once it reaches floor one); if M=1, the elevator should rise from floor one to floor two (and stay there once it reaches floor two). When the elevator is rising, the segments of the display should be sequenced in the order D → G → A (i.e., bottom → middle → top segment); when the elevator is descending, the segments of the display should be sequenced A → G → D (i.e., top → middle → bottom segment).

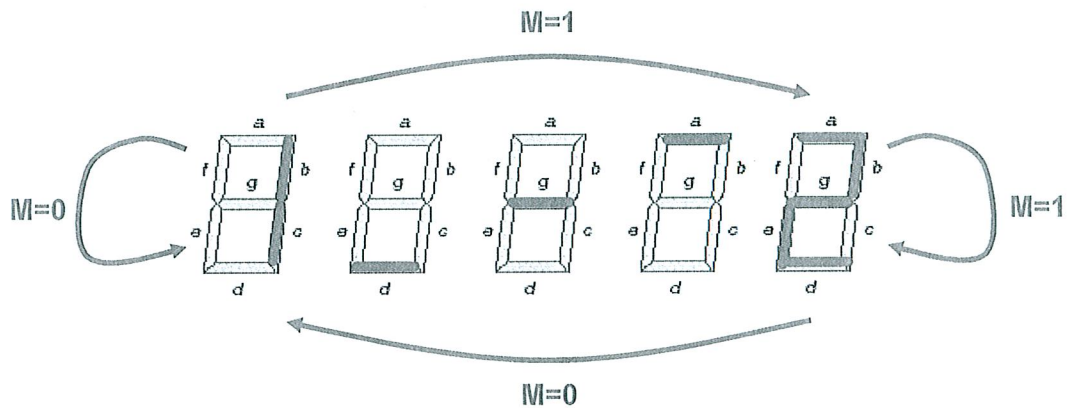The following diagram illustrates the desired mode of operation:



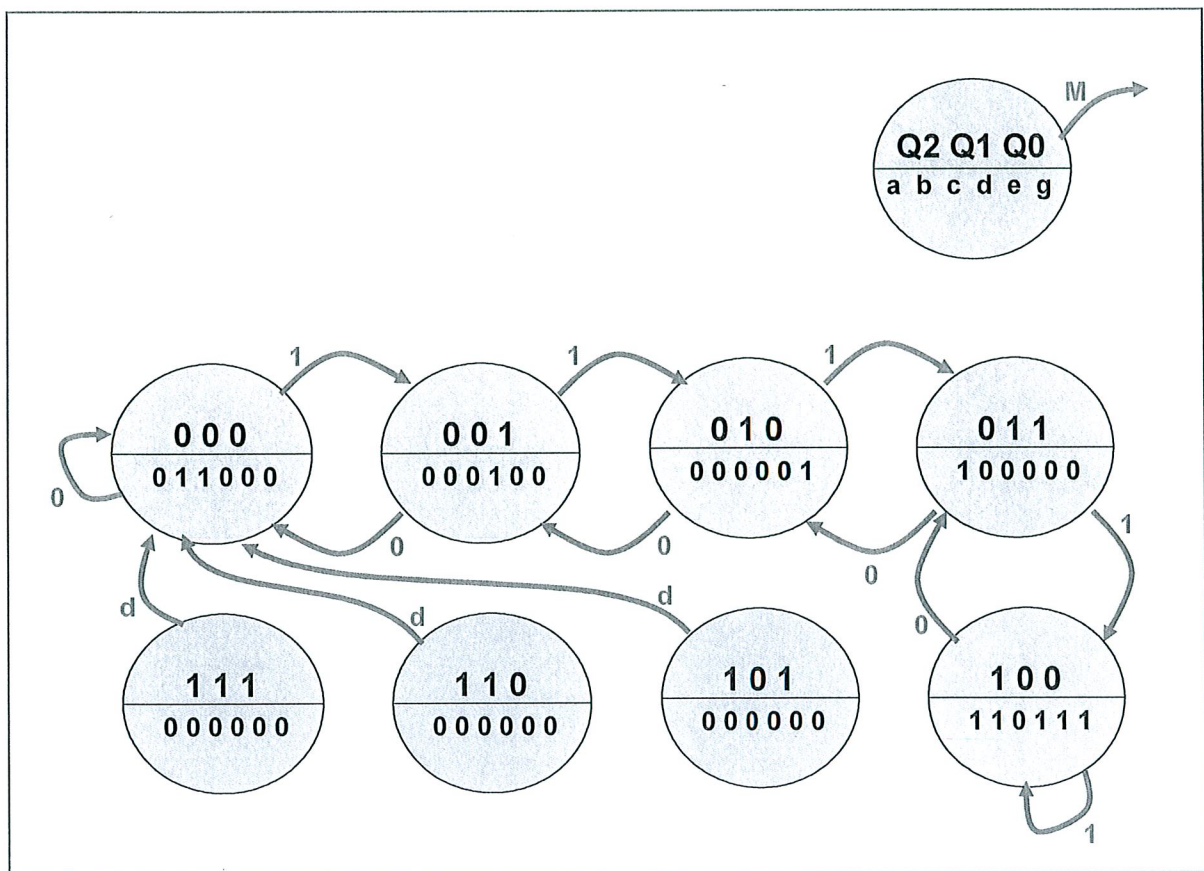Draw a Moore model state transition diagram:




Huddle Board Exercise for Module 3 – No. 4b
Wednesday, March 26, 2014

Complete the state transition diagram, below, for a soda dispensing machine that accepts any combination of nickels, dimes, and quarters which totals \$0.60 (exact change only).

Assume this state machine has the following input signals:

- A – asserted when a nickel is inserted
- B – asserted when a dime is inserted
- C – asserted when a quarter is inserted
- S – asserted when a soda is selected, i.e., the money deposited is "consumed" by the machine, thus resetting the "running total" of the amount entered to zero (and hopefully releasing the desired soft drink)
- R – asserted when the "coin release" option is selected, i.e., the money deposited is released, allowing someone who has entered *too much* money to recover it, also resetting the "running total" of the amount entered to zero

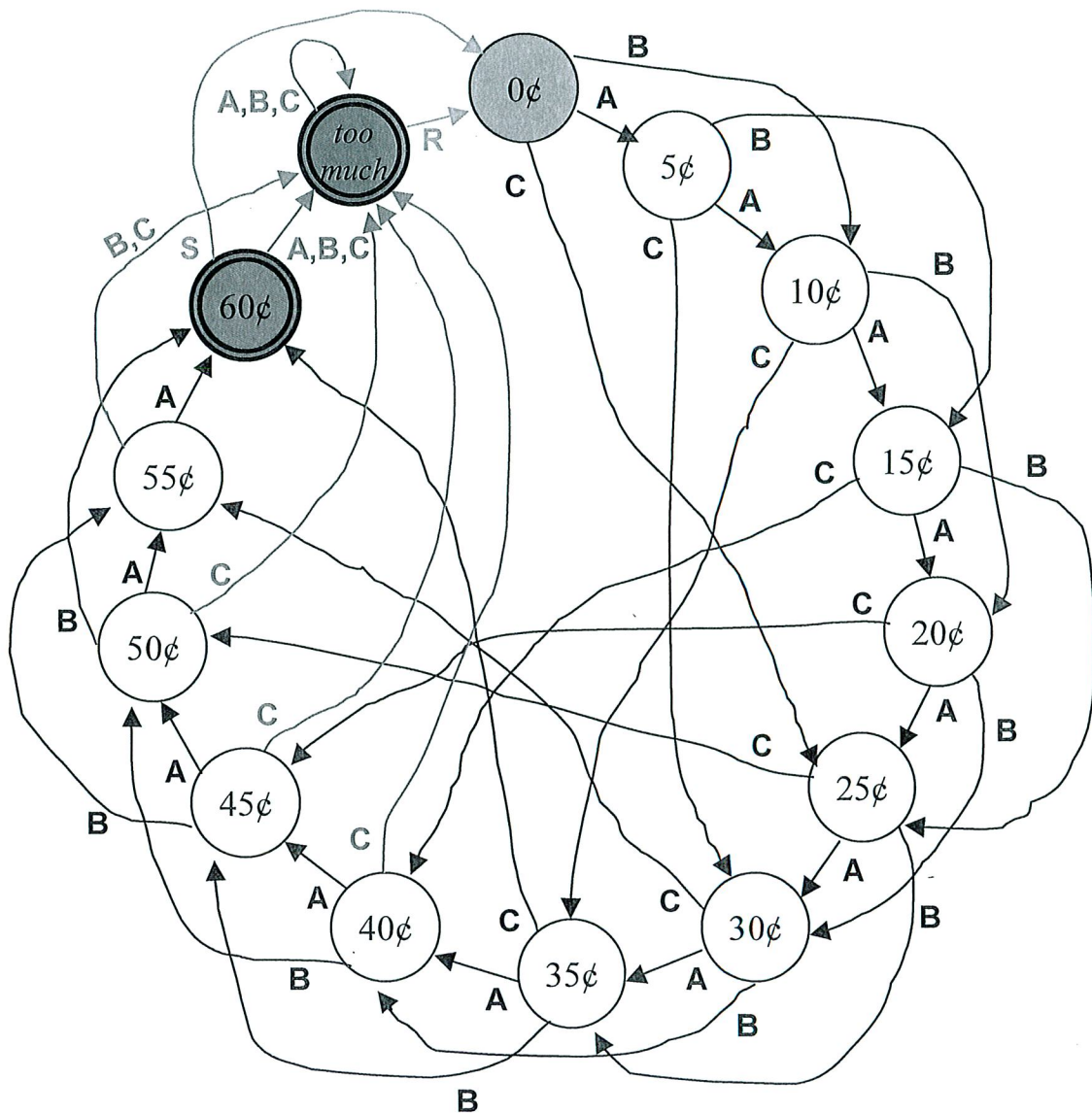


Huddle Board Exercise for Module 3 – No. 5
Wednesday, March 31, 2014

Design a **digital combination lock** that meets the following criteria:

- unlocks when a fixed combination (binary sequence) is entered: 101110
- has three inputs:
 - X – combination data
 - R – relock / reset
 - RESET – asynchronous reset
- has three output signals:
 - LOCKED
 - UNLOCKED
 - ALARM

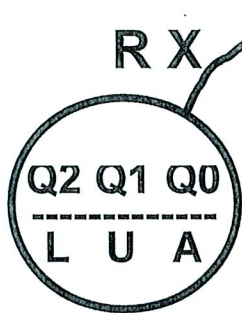Draw a *Moore Model* state transition diagram.



RX

Combination: 101110

