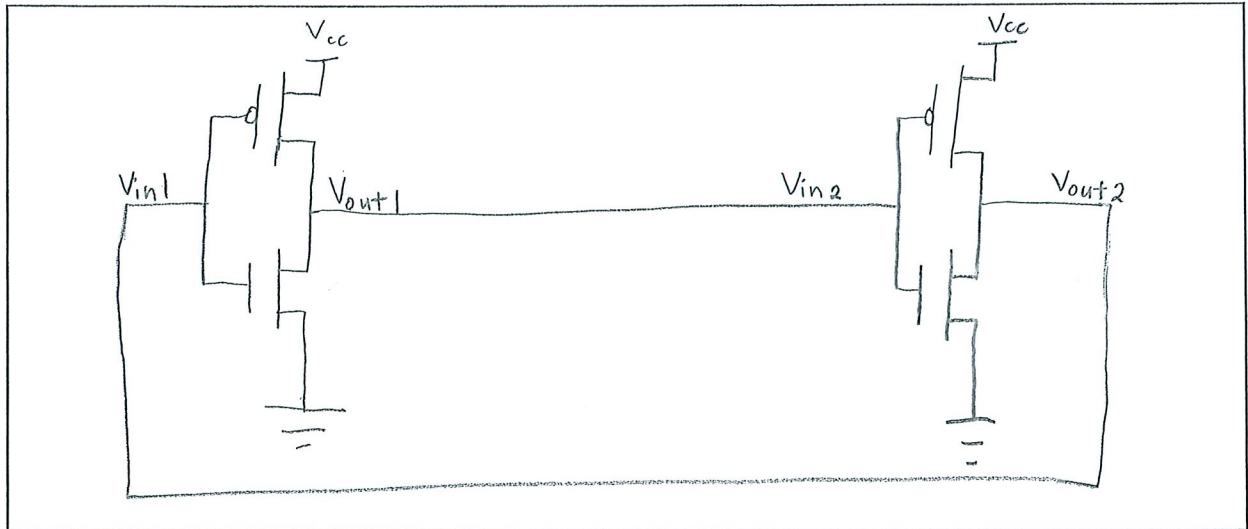


Revisited Concept Exercise for Module 3 – No. 1
Monday, March 10, 2014

1. Draw the circuit for a bi-stable using N- and P-Channel MOSFETs (HINT – consists of two inverters):




2. Define metastability:

The operation of a circuit when it is halfway between a logic '1' voltage and a logic '0' voltage.

3. Fill in the *present state* – *next state* table for an S-R latch (Q^* is the **next state**):


S	R	Q	Q^*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	d
1	1	1	d

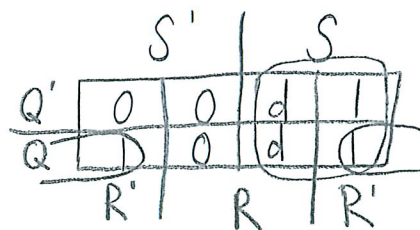

$Q^* = \underline{S + R' \cdot Q}$

Revisited Concept Exercise for Module 3 – No. 2
 Wednesday, March 12, 2014

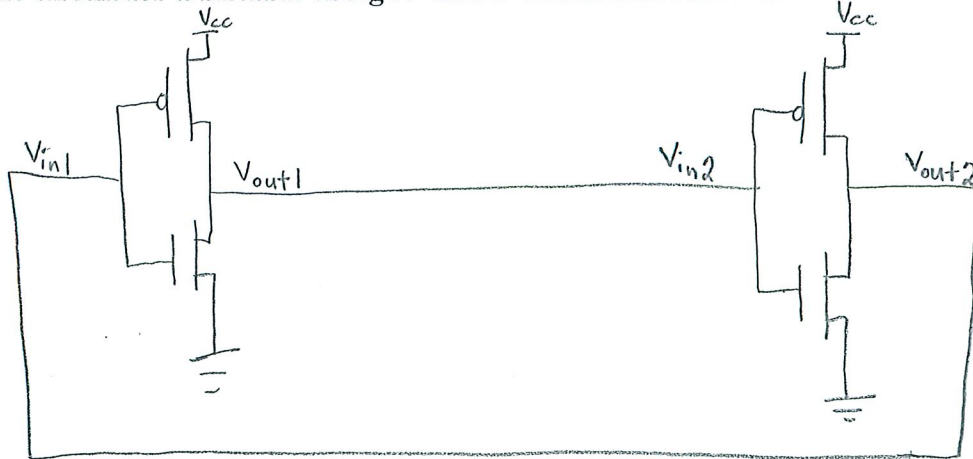1. Draw the circuit for a bistable using N- and P-channel MOSFETs.



2. Fill in the PS-NS table for a “D” flip-flop and derive its next state equation.

D	Q	Q*
0	0	0
0	1	0
1	0	1
1	1	1

	D'	D
Q'	0	1
Q	0	1

$Q^* = \underline{D}$

3. Fill in the PS-NS table for a “T” flip-flop and derive its next state equation.

T	Q	Q*
0	0	0
0	1	1
1	0	1
1	1	0

	T'	T
Q'	0	1
Q	1	0

$Q^* = \underline{T \cdot Q' + T' \cdot Q = T \oplus Q}$

4. Fill in the PS-NS table for an “S-R” flip-flop and derive its next state equation.



S	R	Q	Q*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	d
1	1	1	d

	S'		S	
Q'	0	0	d	1
Q	d	0	d	1
	R'	R	R'	

$Q^* = \underline{S + R' \cdot Q}$



Revisited Concept Exercise for Module 3 – No. 3
Monday, March 24, 2014

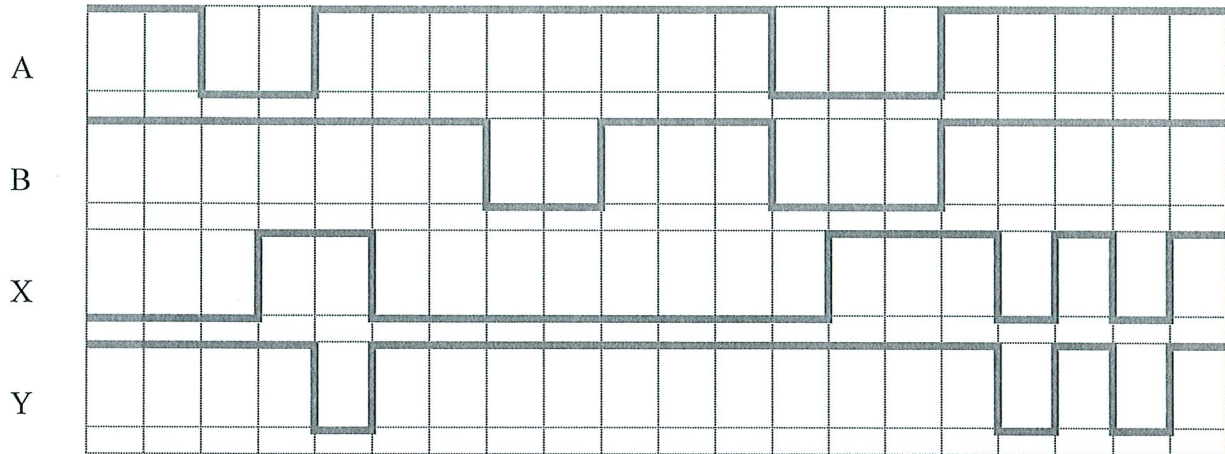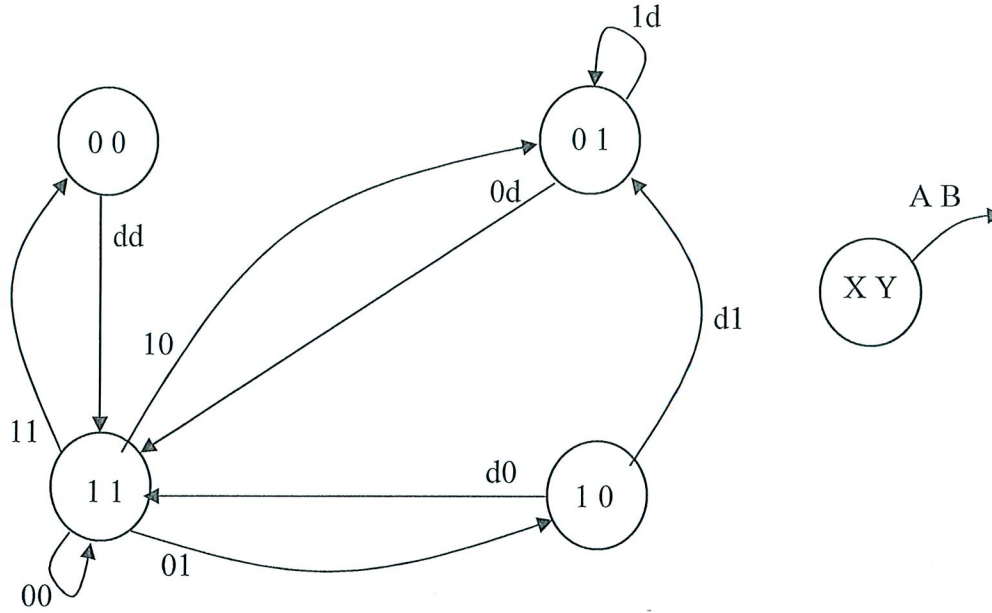Given the following state transition diagram, complete the timing chart below.



Revisited Concept Exercise for Module 3 – No. 4
 Wednesday, March 26, 2014

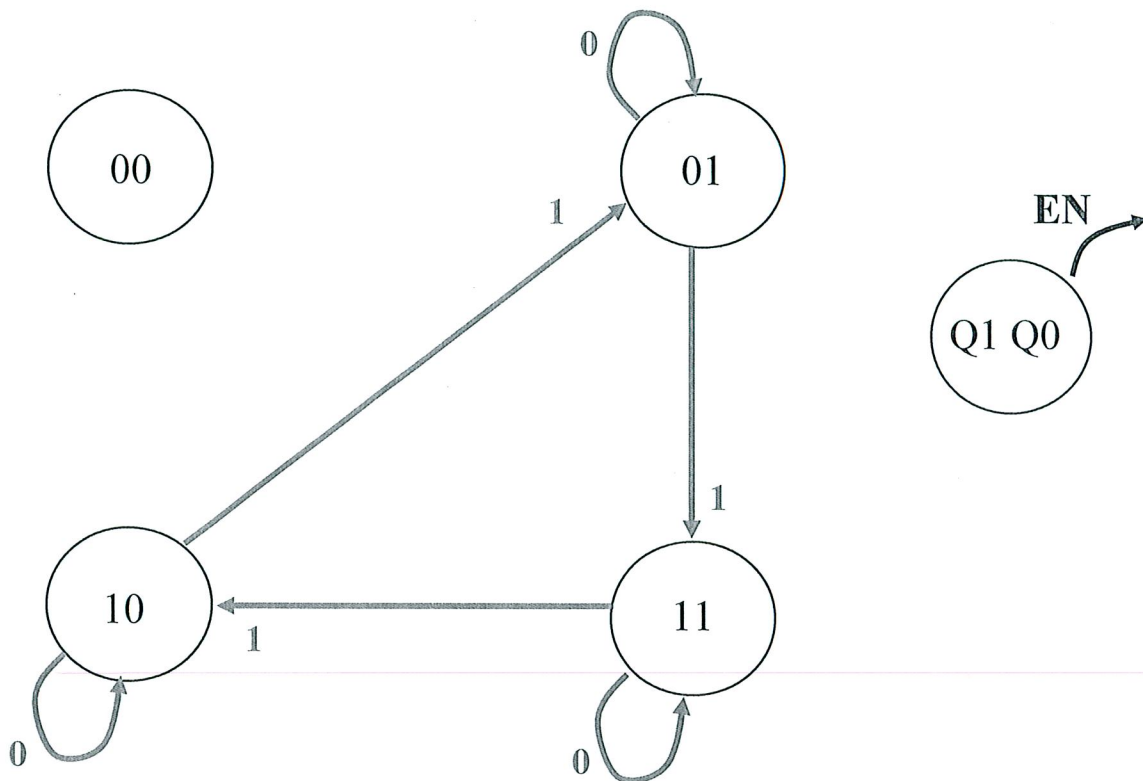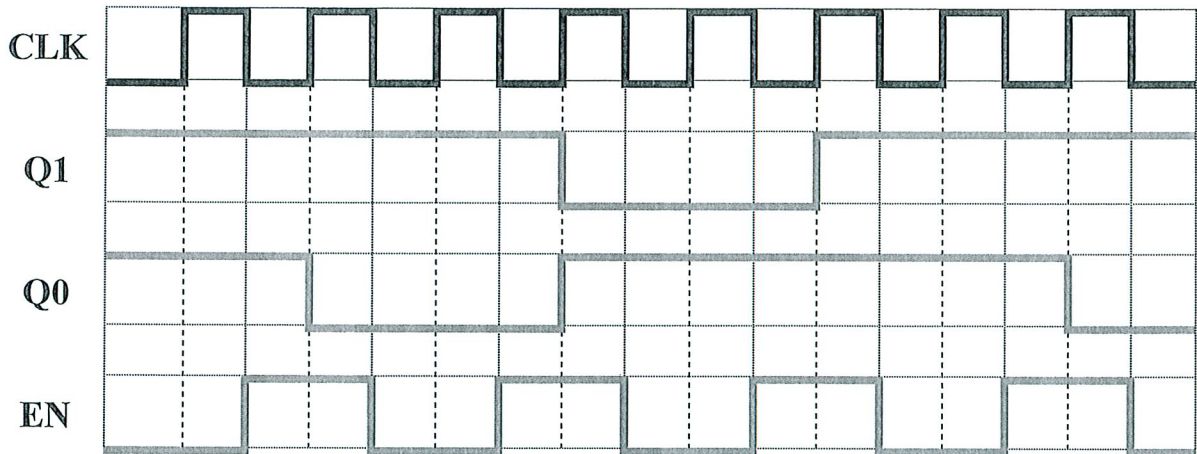Given the timing diagram, below, for a state machine that has one input (EN) and two state variables (Q1 and Q0), derive a state transition diagram (note that there is *one unused state*).



Revisited Concept Exercise for Module 3 – No. 5
 Monday, March 31, 2014

Using a 7-segment display, design a “direction run indicator” (similar to that used on VCRs) that sequences the perimeter segments in a *clockwise* fashion if mode control input $M=1$ ($A \rightarrow B \rightarrow C \rightarrow D \rightarrow E \rightarrow F \rightarrow A \rightarrow B \dots$), or in a *counter-clockwise* fashion if mode control input $M=0$. Input S should control whether the display is running ($S=0$) or stopped ($S=1$); if stopped, the middle segment (G) should be on and the rest should be off. Draw a *Moore* model state transition diagram.

