

Lecture Summary – Module 1

Switching Algebra and CMOS Logic Gates

Learning Outcome: *an ability to analyze and design CMOS logic gates*

Learning Objectives:


- 1-1. convert numbers from one base (radix) to another: 2, 10, 16
- 1-2. define a binary variable
- 1-3. identify the theorems and postulates of switching algebra
- 1-4. describe the principle of duality
- 1-5. describe how to form a complement function
- 1-6. prove the equivalence of two Boolean expressions using perfect induction
- 1-7. describe the function and utility of basic electronic components (resistors, capacitors, diodes, MOSFETs)
- 1-8. define the switching threshold of a logic gate and identify the voltage ranges typically associated with a “logic high” and a “logic low”
- 1-9. define assertion level and describe the difference between a positive logic convention and a negative logic convention
- 1-10. describe the operation of basic logic gates (NOT, NAND, NOR) constructed using N- and P-channel MOSFETs and draw their circuit diagrams
- 1-11. define “fighting” among gate outputs wired together and describe its consequence
- 1-12. define logic gate fan-in and describe the basis for its practical limit
- 1-13. identify key information contained in a logic device data sheet
- 1-14. calculate the DC noise immunity margin of a logic circuit and describe the consequence of an insufficient margin
- 1-15. describe the consequences of a “non-ideal” voltage applied to a logic gate input
- 1-16. describe how unused (“spare”) CMOS inputs should be terminated
- 1-17. describe the relationship between logic gate output voltage swing and current sourcing/sinking capability
- 1-18. describe the difference between “DC loads” and “CMOS loads”
- 1-19. calculate V_{OL} and V_{OH} of a logic gate based on the “on” resistance of the active device and the amount of current sourced/sunk by the gate output
- 1-20. calculate logic gate fan-out and identify a practical lower limit
- 1-21. calculate the value of current limiting resistor needed for driving an LED
- 1-22. describe the deleterious effects associated with loading a gate output beyond its rated specifications
- 1-23. define propagation delay and list the factors that contribute to it
- 1-24. define transition time and list the factors that contribute to it
- 1-25. estimate the transition time of a CMOS gate output based on the “on” resistance of the active device and the capacitive load
- 1-26. describe ways in which load capacitance can be minimized
- 1-27. identify sources of dynamic power dissipation
- 1-28. plot power dissipation of CMOS logic circuits as a function of operating frequency
- 1-29. plot power dissipation of CMOS logic circuits as a function of power supply voltage
- 1-30. describe the function and utility of decoupling capacitors
- 1-31. define hysteresis and describe the operation of Schmitt-trigger inputs
- 1-32. describe the operation and utility of a transmission gate
- 1-33. define high-impedance state and describe the operation of a tri-state buffer
- 1-34. define open drain as it applies to a CMOS logic gate output and calculate the value of pull-up resistor needed
- 1-35. describe how to create “wired logic” functions using open drain logic gates
- 1-36. calculate the value of pull-up resistor needed for an open drain logic gate

Lecture Summary – Module 1-J
Three-State and Open-Drain Outputs


Reference: *Digital Design Principles and Practices* (4th Ed.), pp. 132-136, 138-141

• open-drain outputs

- **definition:** a CMOS output structure that does not include a P-channel (pull-up) transistor is called an *open-drain output*
- an open-drain output is in one of two states: LOW or “open” (i.e., disconnected)
- an *underscored diamond* (or “**O.D.**”) is used to indicate that an output is open drain
- an open-drain output requires an external pull-up resistor to *passively* pull it high in the “open” state (since the output structure does NOT include a P-channel active pull-up)

 


Symbol that denotes an open-drain output

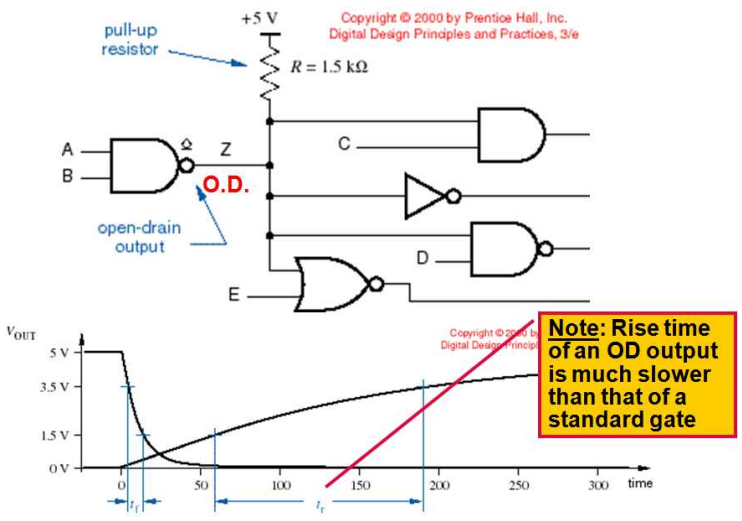


• open-drain outputs, continued...

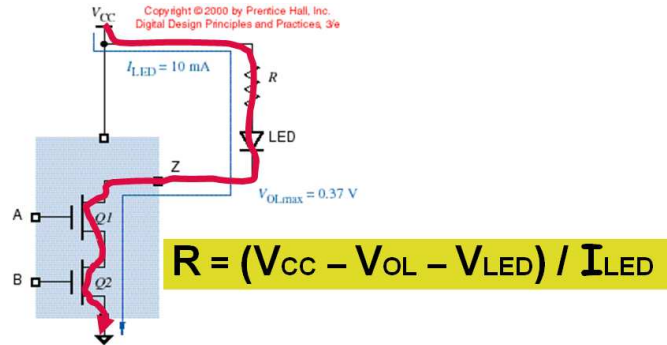- application – driving LEDs (O.D. outputs can typically sink more current than conventional gates)



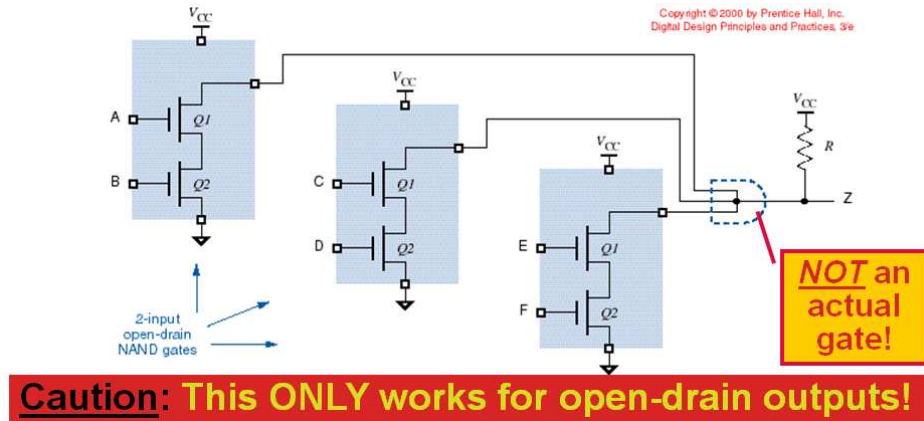
- application - “wired” logic (definition: wired logic is performed if the outputs of several open-drain gates are tied together with a single pull-up resistor)



- pull-up resistor calculations

- in open-drain applications, two calculations bracket the allowable values of the pull-up resistor R:
 - LOW - the sum of the current through R plus the LOW state input currents of the gate inputs driven *must not exceed* the I_{OLmax} of the active device
 - HIGH - the voltage drop across R in the HIGH state *must not reduce* the output voltage below the V_{IHmin} of the driven gate inputs

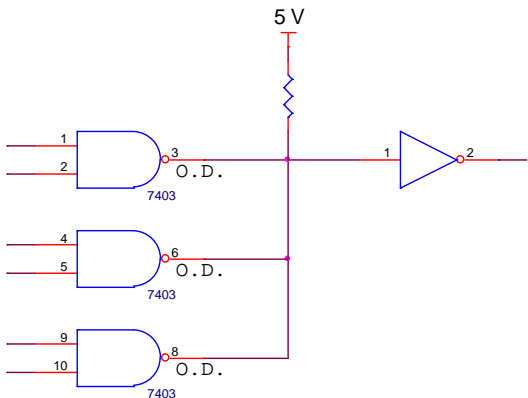
- example: calculate a suitable value of pull-up resistor to use with the following circuit:



Specifications (hypothetical data):

- Off-state leakage current of O.D. NAND gate output: $+3 \mu A$
- I_{IH} and I_{IL} required by inverter input: $\pm 1 \mu A$
- V_{IH} desired for inverter input: 4.9 V
- I_{OLmax} of O.D. NAND gate output: $+10 \text{ mA}$ @ $V_{OL} = 0.3 \text{ V}$

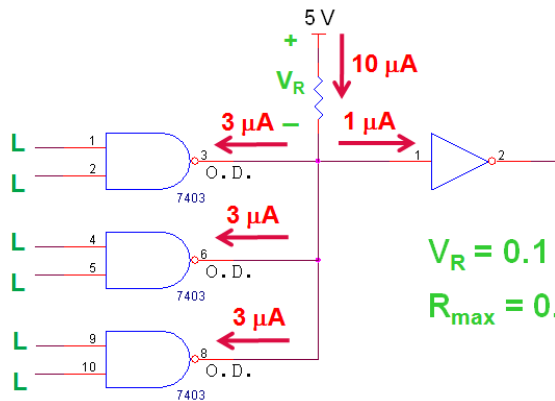- open-drain outputs, continued...
 - pull-up resistor calculation example, continued...
 - solution, maximum R Value – based on V_{IH} desired




Conclusion – A pull-up resistor ranging from 470Ω (R_{min}) to $10,000 \Omega$ (R_{max}) will satisfy the specified constraints

$V_R = 0.1 \text{ V}$ $I_R = 10 \mu\text{A}$
 $R_{max} = 0.1/0.00001 = 10,000 \Omega$

- solution, minimum R Value – based on I_{OLmax} of one gate

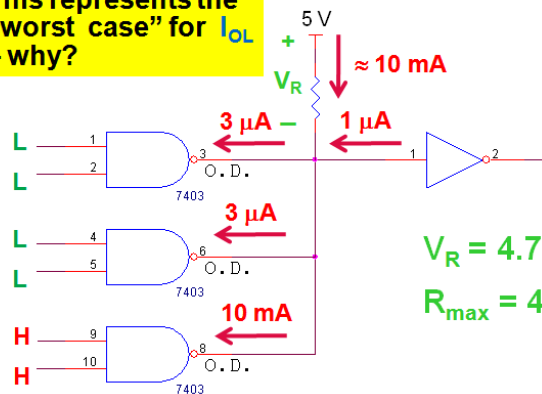This represents the “worst case” for I_{OL} – why?




Here, can safely ignore leakage and I_{IL} currents – why?

$V_R = 4.7 \text{ V}$ $I_R \approx 10 \text{ mA}$
 $R_{min} = 4.7/0.01 = 470 \Omega$

NOTE: Picking R_{min} will minimize the rise time, while picking R_{max} will minimize the power dissipation

- “prove” the “worst case” scenario ($R = 470 \Omega$)

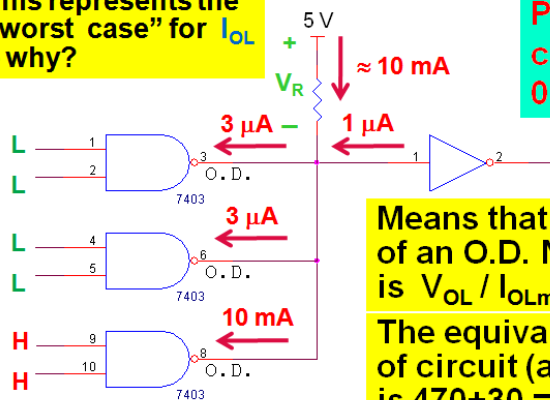This represents the “worst case” for I_{OL} – why?



Power dissipation of circuit is $I_R^2 \times R_{eq} = 0.01^2 \times 500 \approx 50 \text{ mW}$


Means that the “on” resistance of an O.D. NAND gate used here is $V_{OL} / I_{OLmax} = 0.3/0.01 = 30 \Omega$

The equivalent load impedance of circuit (across power supply) is $470+30 = 500 \Omega$

Specifications (hypothetical data):

- Off-state leakage current of O.D. NAND gate output: $+3 \mu\text{A}$
- I_{IH} and I_{IL} required by inverter input: $\pm 1 \mu\text{A}$
- V_{IH} desired for inverter input: 4.9 V
- I_{OLmax} of O.D. NAND gate output: $+10 \text{ mA @ } V_{OL} = 0.3 \text{ V}$

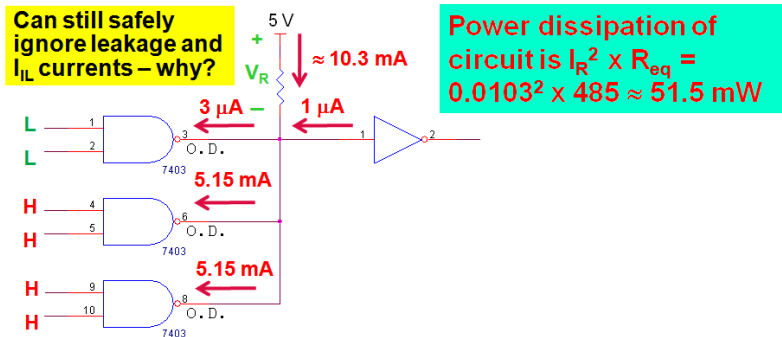- open-drain outputs, continued...
 - pull-up resistor calculation example, continued...
 - “proof”, continued...




Next, turn on two O.D. gates

The equivalent load impedance of circuit is $470 + 15 = 485 \Omega$ (because have **two** 30Ω “on” resistances in parallel)

I_R is now $5 / 485 = 0.0103 \text{ A} = 10.3 \text{ mA}$, which is split between the two gates that are “on”

▪ conclusions

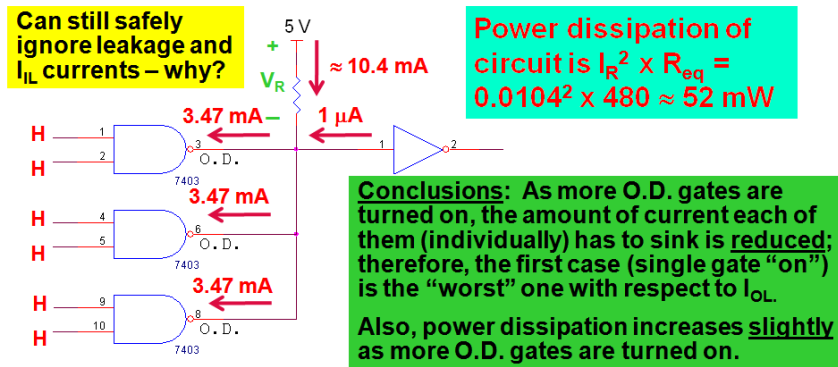


Finally, turn on all three O.D. gates


The equivalent load impedance of circuit is $470 + 10 = 480 \Omega$ (because have **three** 30Ω “on” resistances in parallel)

I_R is now $5 / 480 = 0.0104 \text{ A} = 10.4 \text{ mA}$, which is split among the three gates that are “on”

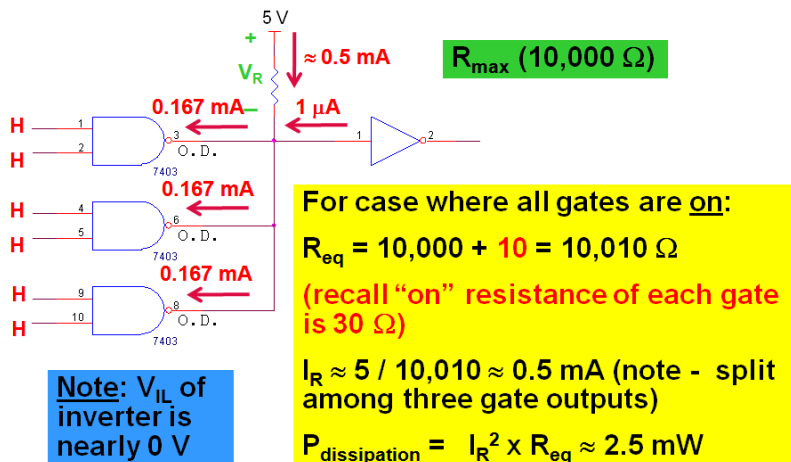
- compare power dissipation of circuit using R_{min} vs. R_{max} as the pull-up resistor



 - open-drain outputs, continued...
 - pull-up resistor calculation example, continued...
 - power dissipation comparison, continued...



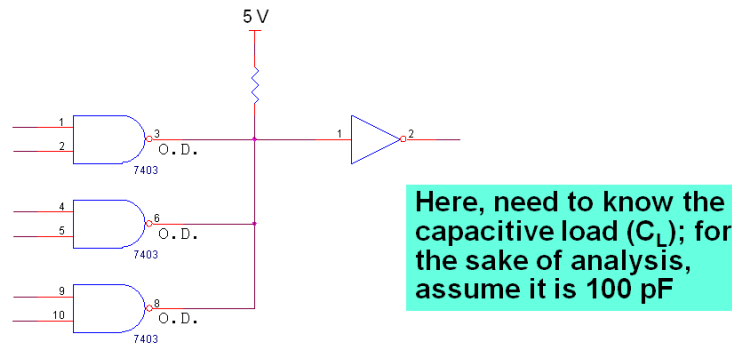
- compare rise time estimates of circuit using Rmin vs. Rmax as the pull-up resistor



Comparison:

- For Rmin, rise time estimate is $470 \times 100 \times 10^{-12} = 47 \text{ ns}$
- For Rmax, rise time estimate is $10,000 \times 100 \times 10^{-12} = 1000 \text{ ns}$
- Conclusion: rise time for Rmax case is considerably longer

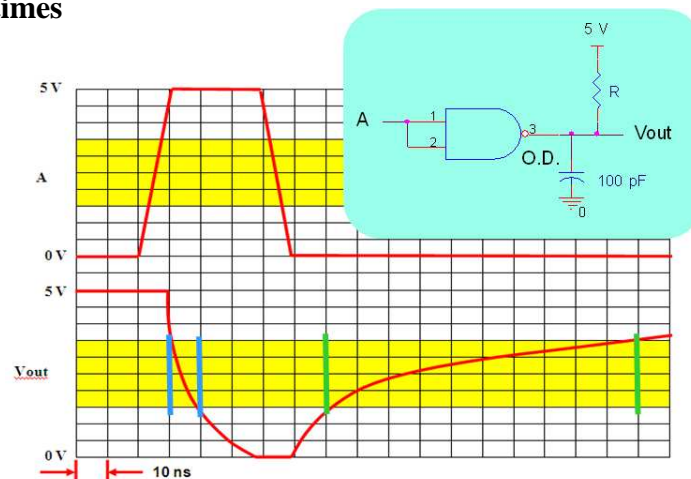- example: estimate the “on” resistance of an O.D. gate and pull-up resistor value based on rise/fall times



$\text{rise time} = 100 \text{ ns} = R_{\text{pull-up}} \times 100 \text{ pF} \rightarrow R_{\text{pull-up}} = 1000 \Omega$
 $\text{fall time} = 10 \text{ ns} = R_{\text{on}} \times 100 \text{ pF} \rightarrow R_{\text{on}} = 100 \Omega$