

**Revisited Concept Exercise for Module 1 – No. 1**  
**Wednesday, January 15, 2014**

➤ **Convert  $(1101101)_2$  to base 10**

➤ **Convert  $(3487)_{10}$  to base 16**

➤ **Convert  $(C29E)_{16}$  to base 2**

➤ **Convert  $(1101101)_2$  to base 16**



**Revisited Concepts Exercise for Module 1 – No. 2a**  
**Friday, January 17, 2014**

**MATCHING – Write the letter of the example (on the right) corresponding to the named axiom or theorem:**

___ <b>Involution</b>	<b>A.</b> $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$
___ <b>Idempotency</b>	<b>B.</b> $X + Y = Y + X$
___ <b>Identity</b>	<b>C.</b> $X \cdot Y + X \cdot Y' = X$
___ <b>Null Element</b>	<b>D.</b> $X \cdot X \cdot X = X$
___ <b>Complement</b>	<b>E.</b> $X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$
___ <b>Associativity</b>	<b>F.</b> $X + 1 = 1$
___ <b>Commutivity</b>	<b>G.</b> $X \cdot X' = 0$
___ <b>Distributivity</b>	<b>H.</b> $(X + Y)' = X' \cdot Y'$
___ <b>Combining</b>	<b>I.</b> $(X')' = X$
___ <b>DeMorgan's Law</b>	<b>J.</b> $X + 0 = X$
___ <b>Consensus</b>	<b>K.</b> $X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$



**Revisited Concepts Exercise for Module 1 – No. 2b**  
**Friday, January 17, 2014**

**MATCHING – Write the letter of the description (on the right) corresponding to the concept or device:**

- |                                       |  |
|---------------------------------------|--|
| ___ Capacitor                         | A. Difference in electrical potential  |
| ___ Computer                          | B. The flow of charge in a conductor between two points having a difference in potential   |
| ___ Current                           | C. Amount of energy  |
| ___ Forward Voltage                   | D. A device that stores an electric charge   |
| ___ Integrated Circuit (IC or “Chip”) | E. The voltage drop across a Light Emitting Diode when it is forward biased  |
| ___ Microcontroller                   | F. A collection of logic gates and/or other electronic circuits fabricated on a single silicon chip  |
| ___ Microprocessor                    | G. An integrated circuit onto which a generic logic circuit can be programmed  |
| ___ Power                             | H. A digital device that sequentially executes a stored program  |
| ___ Programmable Logic Device (PLD)   | I. A single-chip embodiment of the major functional blocks of a computer   |
| ___ Voltage                           | J. A complete computer on a chip, including integrated peripherals   |
| ___ CMOS                              | K. Fiberglass reinforced epoxy substrate with etched copper circuitry (typically in multiple layers) used to create virtually all electronic devices   |
| ___ Discrete Logic                    | L. A circuit constructed using small-scale Integrated (SSI) and medium-scale integrated (MSI) logic devices (NAND gates, decoders, Multiplexers, etc.) |
| ___ Printed Circuit Board (PCB)       | M. A silicon chip fabrication technology based on Use of complementary pairs of NMOS and PMOS field effect transistors (MOSFETs)                       |



**Revisited Concepts Exercise for Module 1 – No. 3**  
**Wednesday, January 22, 2014**

1. Describe the function of a P-channel MOSFET:
  
  
  
  
  
  
  
  
  
  
2. When a MOSFET is off, its drain-to-source impedance is on the order of:
  
  
  
  
  
  
  
  
  
  
3. Describe the function of a combinational circuit:
  
  
  
  
  
  
  
  
  
  
4. Fill out the truth table for a **NOT** gate:


A	(A)'
0	
1	

5. If I'm on a deserted island with my DK-1 kit (starring on the *Digital Survivor* show), I can build "anything digital" using only a bucket full of what (single) type of 2-input logic gate? What is the name of the property upon which this premise is based?

Type of 2-input gate: \_\_\_\_\_

Name of property: \_\_\_\_\_

 6. Using a total of **three** N-channel MOSFETs and **three** P-channel MOSFETs, draw a circuit schematic for a **three-input NAND** gate. The gate inputs should be labeled A, B, C and the gate output should be labeled F. Be sure to show the power (Vcc) and ground (GND) connections as well.






**Revisited Concepts Exercise for Module 1 - No. 4**  
**Monday, January 27, 2014**

1. Fill out the truth table for a **2-input NAND** gate:

A	B	$(A \cdot B)'$
0	0	
0	1	
1	0	
1	1	

 2. Draw a MOSFET-level circuit for a **2-input NAND** gate:





**Revisited Concepts Exercise for Module 1 – No. 5**  
**Wednesday, January 29, 2014**

1. Is it possible to have a negative DCNM? If so, what would it mean?
  
  
  
  
  
  
  
  
  
  
2. What is the minimum DCNM necessary to ensure a functional circuit?
  
  
  
  
  
  
  
  
  
  
3. Is it possible to have a negative fan-out? If so, what would it mean?
  
  
  
  
  
  
  
  
  
  
4. What is the minimum fan-out necessary to ensure a functional circuit?
  
  
  
  
  
  
  
  
  
  
5. What is the factor that limits the practical fan-in of a CMOS logic gate?



**Revisited Concepts Exercise for Module 1 – No. 6**  
**Friday, January 31, 2014**

Assume hypothetical logic family has the following D.C. characteristics:

$V_{CC} = 5\text{ V}$	$V_{OH} = 3.50\text{ V}$	$V_{OL} = 0.50\text{ V}$	$V_{IH} = 2.50\text{ V}$	$V_{IL} = 1.00\text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -5.0\text{ mA}$	$I_{OL} = 10\text{ mA}$	$I_{IH} = 500\text{ }\mu\text{A}$	$I_{IL} = -2.0\text{ mA}$

When interfacing an *LED* that has a *forward voltage* of *1.5 V* to this logic family in a *current sourcing* configuration, *maximum brightness* will be achieved (within the rated specifications) using a current limiting resistor of the value along with its power dissipation:

Circuit and calculations:

Current limiting resistor = \_\_\_\_\_  $\Omega$     Resistor power dissipation = \_\_\_\_\_ mW

When interfacing an *LED* that has a *forward voltage* of *1.5 V* to this logic family in a *current sinking* configuration, *maximum brightness* will be achieved (within the rated specifications) using a current limiting resistor of the value along with its power dissipation:

Circuit and calculations:

Current limiting resistor = \_\_\_\_\_  $\Omega$     Resistor power dissipation = \_\_\_\_\_ mW

Practice for standardized exam questions — determine the one best response.

1. When a gate's rated  $I_{OH}$  specification is *exceeded*, the following is likely to happen:  
(A) the  $V_{OH}$  of the gate will increase and the  $t_{TLH}$  of the gate will decrease  
(B) the  $V_{OH}$  of the gate will decrease and the  $t_{TLH}$  of the gate will increase  
(C) the  $V_{OL}$  of the gate will increase and the  $t_{THL}$  of the gate will increase  
(D) the  $V_{OL}$  of the gate will decrease and the  $t_{THL}$  of the gate will decrease  
(E) none of the above
2. When a gate's rated  $I_{OL}$  specification is *exceeded*, the following is likely to happen:  
(A) the  $V_{OH}$  of the gate will increase and the  $t_{TLH}$  of the gate will decrease  
(B) the  $V_{OH}$  of the gate will decrease and the  $t_{TLH}$  of the gate will increase  
(C) the  $V_{OL}$  of the gate will increase and the  $t_{THL}$  of the gate will increase  
(D) the  $V_{OL}$  of the gate will decrease and the  $t_{THL}$  of the gate will decrease  
(E) none of the above
3. For CMOS gates,  $V_{IHmin}$  is typically:  
(A) 10% of the supply voltage ( $V_{cc}$ )  
(B) 30% of the supply voltage ( $V_{cc}$ )  
(C) 50% of the supply voltage ( $V_{cc}$ )  
(D) 70% of the supply voltage ( $V_{cc}$ )  
(E) 90% of the supply voltage ( $V_{cc}$ )
4. For CMOS gates, the *switching threshold* is typically:  
(A) 10% of the supply voltage ( $V_{cc}$ )  
(B) 30% of the supply voltage ( $V_{cc}$ )  
(C) 50% of the supply voltage ( $V_{cc}$ )  
(D) 70% of the supply voltage ( $V_{cc}$ )  
(E) 90% of the supply voltage ( $V_{cc}$ )
5. The largest source of noise in a digital circuit is from:  
(A) RF communication devices (e.g., cell phones)  
(B) cosmic rays  
(C) power line disturbances  
(D) the logic gates themselves  
(E) none of the above
6. *Electromagnetic interference* could cause a “floating” (unconnected) gate input to:  
(A) change from high-to-low or from low-to-high  
(B) increase the  $V_{IH}$  of the gate relative to its specified value  
(C) decrease the  $V_{IL}$  of the gate relative to its specified value  
(D) pick up the satellite broadcast of a Purdue basketball victory  
(E) none of the above