

Huddle Board Exercise for Module 4 – No. 1a

Monday, April 14, 2014

Complete the following ABEL file so that it implements a 4-bit *carry look-ahead* adder based on the DECLARATIONS section provided below.

```
MODULE cla4
TITLE '4-bit Carry Look-Ahead Adder'
```

DECLARATIONS

```
X0..X3, Y0..Y3 pin; " operands
CIN pin; " carry in
S0..S3 pin istype 'com'; " sum outputs
C0..C3 pin istype 'com'; " carry outputs (C3 is carry out)
P0..P3 pin istype 'com'; " propagate functions
```

```
G0 = X0&Y0; " generate functions
G1 = X1&Y1;
G2 = X2&Y2;
G3 = X3&Y3;
```

$$\begin{array}{r}
 C2 \quad C1 \quad C0 \quad CIN \\
 X3 \quad X2 \quad X1 \quad X0 \\
 + \quad Y3 \quad Y2 \quad Y1 \quad Y0 \\
 \hline
 C3 \quad S3 \quad S2 \quad S1 \quad S0
 \end{array}$$

EQUATIONS

```
P0 = X0$Y0; " propagate functions
P1 = X1$Y1;
P2 = X2$Y2;
P3 = X3$Y3;
```

" carry functions

```
C0 = _____ G0 # CIN&P0 ;
```

```
C1 = _____ G1 # G0&P1 # CIN&P0&P1 ;
```

```
C2 = _____ G2 # G1&P2 # G0&P1&P2 # CIN&P0&P1&P2 ;
```

```
C3 = _____ G3 # G2&P3 # G1&P2&P3 # G0&P1&P2&P3 # CIN&P0&P1&P2&P3 ;
```


```
S0 = CIN$P0; " sum functions
S1 = C0$P1;
S2 = C1$P2;
S3 = C2$P3;
```

```
END
```

Huddle Board Exercise for Module 4 – No. 1b

Monday, April 14, 2014

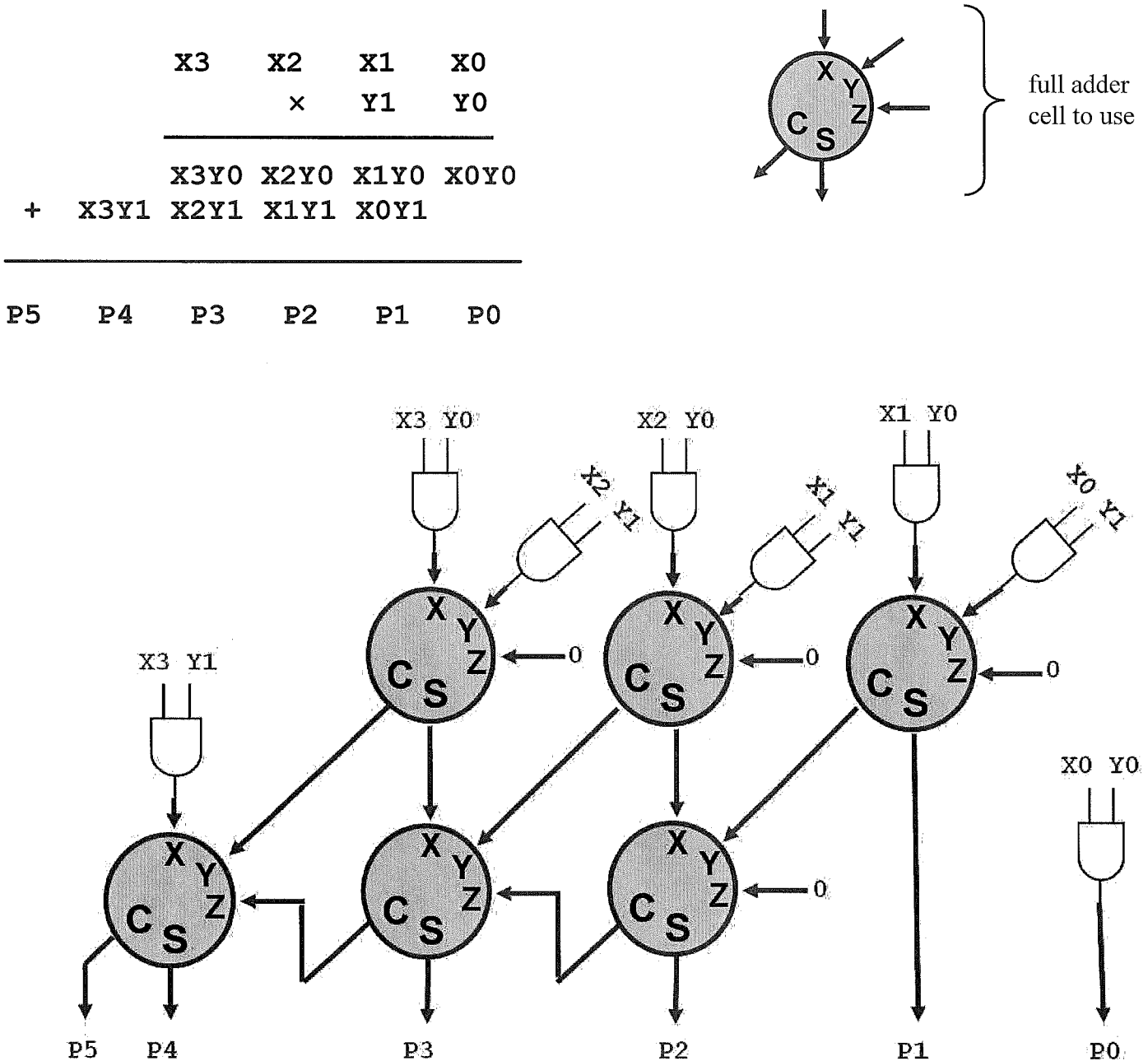Draw a circuit that multiplies a 4-bit unsigned binary number $X_3 X_2 X_1 X_0$ by a 2-bit unsigned binary number $Y_1 Y_0$, using an array of full-adder cells. Determine the worst case propagation delay if each full adder takes 10 ns to produce its C and S outputs, and each AND gate (used to generate the product components) has 5 ns of propagation delay.




The worst case propagation delay is: 45 ns.

Huddle Board Exercise for Module 4 – No. 2a
 Wednesday, April 16, 2014

Assume the simple computer instruction set has been changed to the following:

Opcode	Mnemonic	Function Performed
0 0 0	ADD <i>addr</i>	Add contents of <i>addr</i> to contents of A
0 0 1	SUB <i>addr</i>	Subtract contents of <i>addr</i> from contents of A
0 1 0	LDA <i>addr</i>	Load A with contents of location <i>addr</i>
0 1 1	XOR <i>addr</i>	XOR contents of <i>addr</i> with contents of A
1 0 0	STA <i>addr</i>	Store contents of A at location <i>addr</i>
1 0 1	HLT	Halt – Stop, discontinue execution

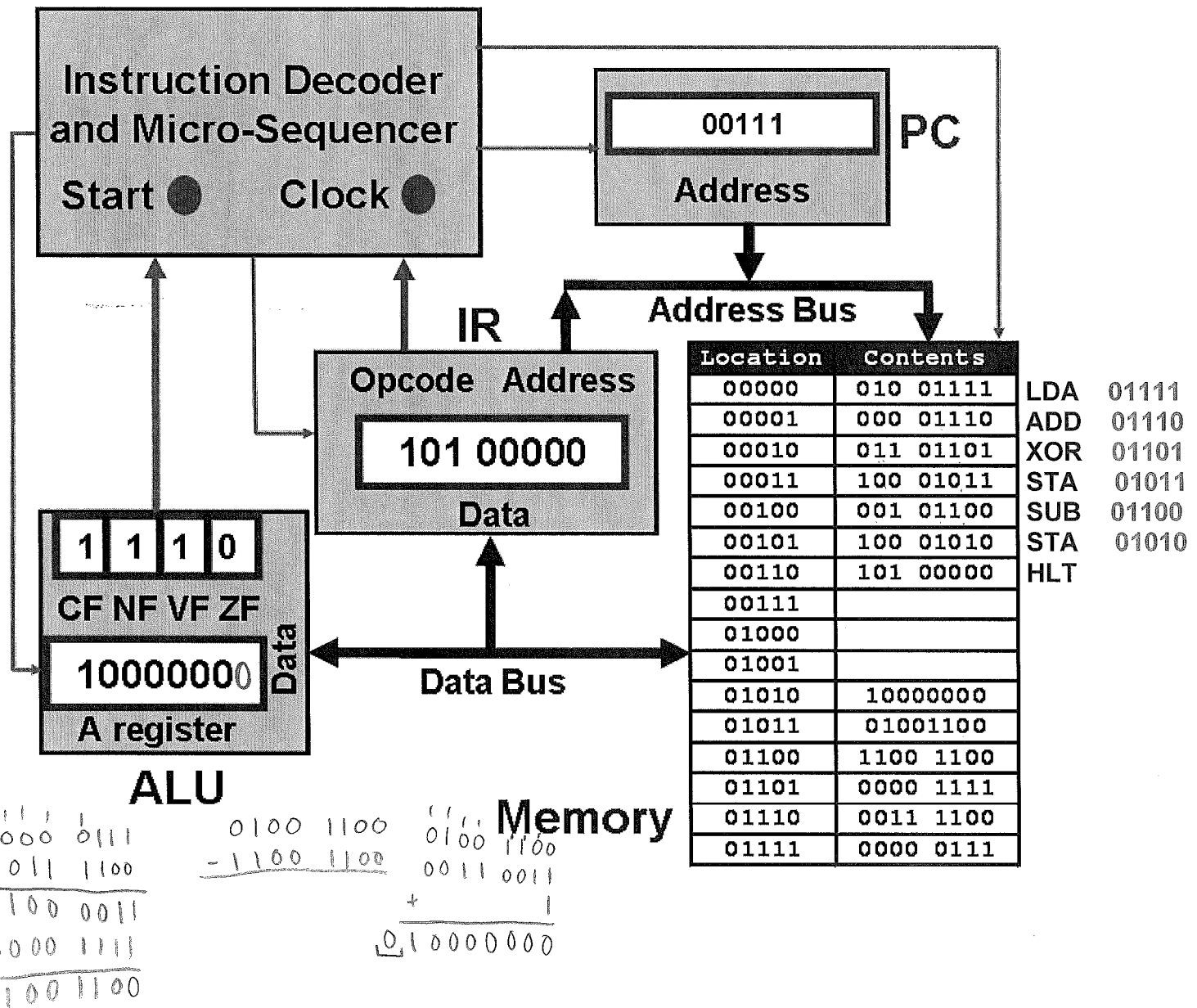On the instruction trace worksheet, below, show the *final result* of executing the program stored in memory *up to and including* the HLT instruction.



Huddle Board Exercise for Module 4 – No. 2b
Wednesday, April 16, 2014

From the **BLOCK DIAGRAM** for one bit (“i”) of the ALU, complete the table below:

AOE	ALE	ALX	ALY	Function Performed	CF	ZF	NF	VF
0	1	0	0	LDA: $[Q3..Q0] \leftarrow [D3..D0]$	•	X	X	•
0	1	0	1	AND: $[Q3..Q0] \leftarrow [Q3..Q0] \cap [D3..D0]$	•	X	X	•
0	1	1	0	SUB: $[Q3..Q0] \leftarrow [Q3..Q0] - [D3..D0]$	X	X	X	X
0	1	1	1	ADD: $[Q3..Q0] \leftarrow [Q3..Q0] + [D3..D0]$	X	X	X	X
1	0	d	d	OUT: $[D3..D0] \leftarrow [Q3..Q0]$	•	•	•	•
0	0	d	d	(no operation – retain state)	•	•	•	•

“X” indicates the flag is affected by the function performed, “•” indicates the flag is not affected

