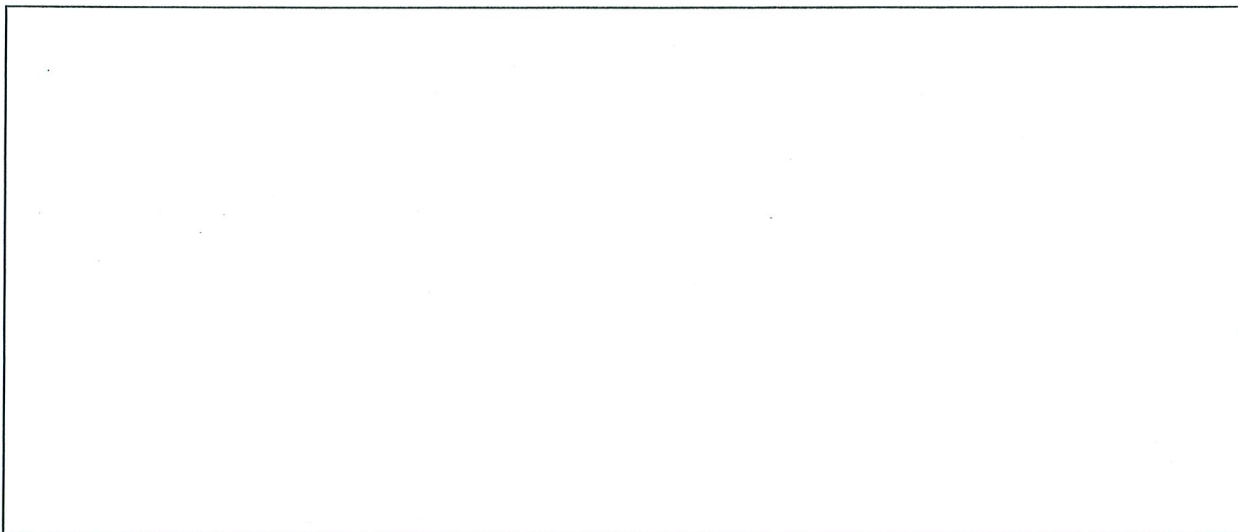


**Revisited Concept Exercise for Module 3 – No. 1**  
**Monday, March 10, 2014**

1. Draw the circuit for a bi-stable using N- and P-Channel MOSFETs (HINT – consists of two inverters):



2. Define metastability:

---

---

3. Fill in the *present state* – *next state* table for an S-R latch ( $Q^*$  is the **next state**):

S	R	Q	$Q^*$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

$Q^* =$  \_\_\_\_\_



**Revisited Concept Exercise for Module 3 – No. 2**  
**Wednesday, March 12, 2014**

1. Draw the circuit for a bistable using N- and P-channel MOSFETs.

2. Fill in the PS-NS table for a “D” flip-flop and derive its next state equation.

D	Q	Q*
0	0	
0	1	
1	0	
1	1	

$$Q^* = \underline{\hspace{2cm}}$$

3. Fill in the PS-NS table for a “T” flip-flop and derive its next state equation.

T	Q	Q*
0	0	
0	1	
1	0	
1	1	

$$Q^* = \underline{\hspace{2cm}}$$



4. Fill in the PS-NS table for an “S-R” flip-flop and derive its next state equation.

S	R	Q	Q*
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

$$Q^* = \underline{\hspace{2cm}}$$







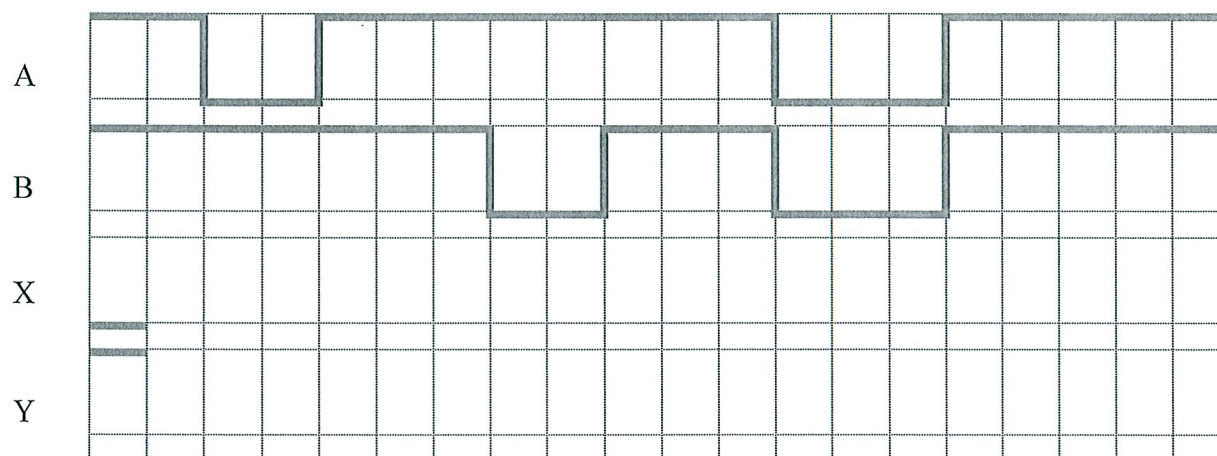
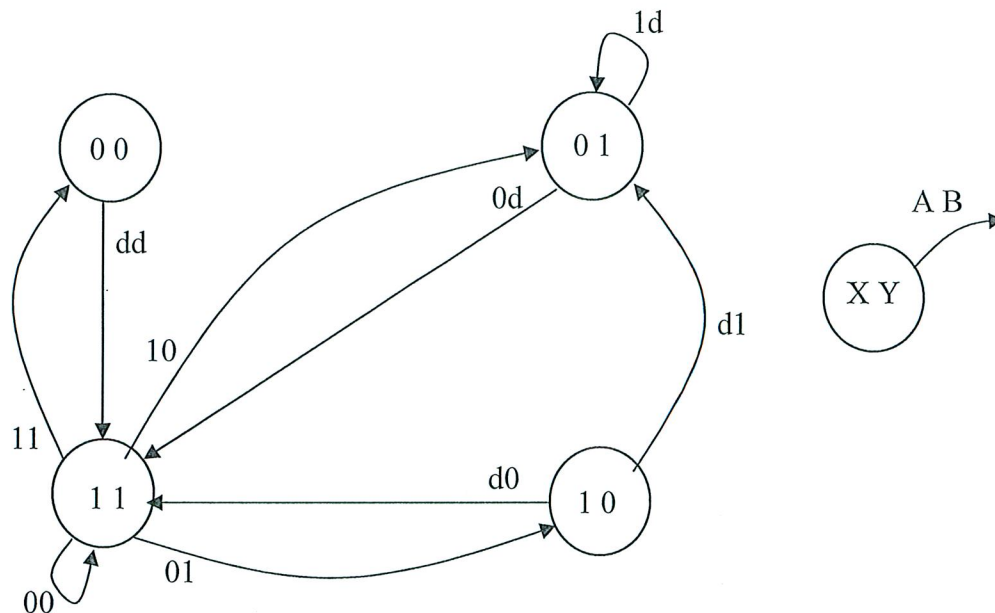
**Given the following state transition diagram, complete the timing chart below.**





**Revisited Concept Exercise for Module 3 – No. 4**  
**Wednesday, March 26, 2014**

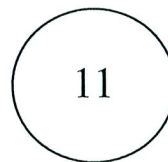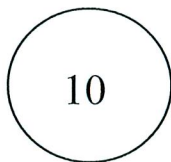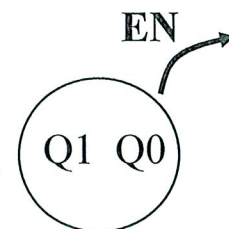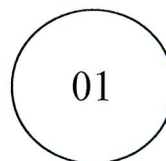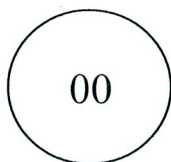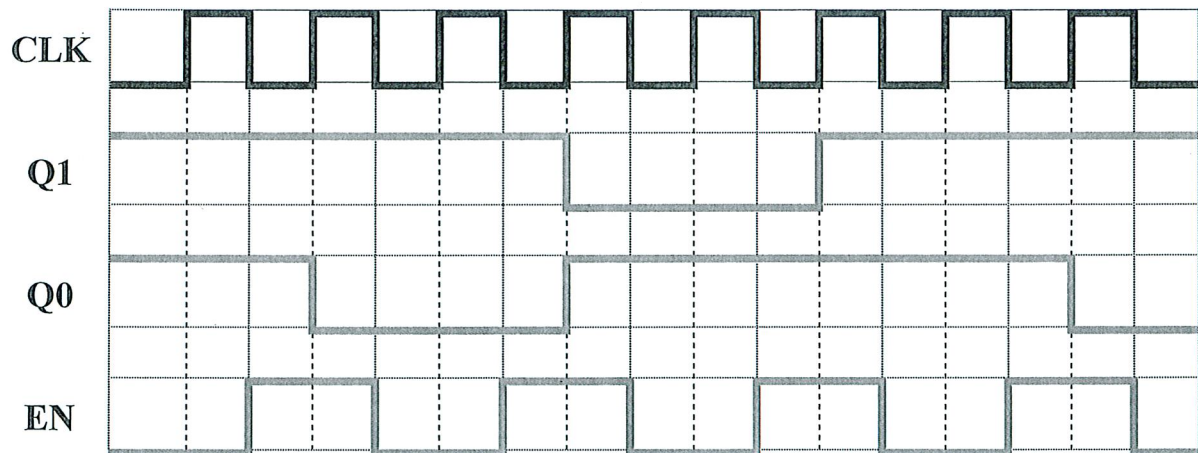Given the timing diagram, below, for a state machine that has one input (EN) and two state variables (Q1 and Q0), derive a state transition diagram (note that there is *one unused state*).







**Revisited Concept Exercise for Module 3 – No. 5**  
**Monday, March 31, 2014**

Using a 7-segment display, design a “direction run indicator” (similar to that used on VCRs) that sequences the perimeter segments in a *clockwise* fashion if mode control input  $M=1$  ( $A \rightarrow B \rightarrow C \rightarrow D \rightarrow E \rightarrow F \rightarrow A \rightarrow B \dots$ ), or in a *counter-clockwise* fashion if mode control input  $M=0$ . Input  $S$  should control whether the display is running ( $S=0$ ) or stopped ( $S=1$ ); if stopped, the middle segment ( $G$ ) should be on and the rest should be off. Draw a *Moore* model state transition diagram.

