

Revisited Concept Exercises for Module 2 – No. 1
Monday, February 17, 2014

Given the truth table, below, determine the following:

X	Y	Z	F(X,Y,Z)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


F(X,Y,Z) expressed as:

an *on-set*: _____

an *off-set*: _____

Revisited Concept Exercise for Module 2 – No. 1a
Monday, February 17, 2014

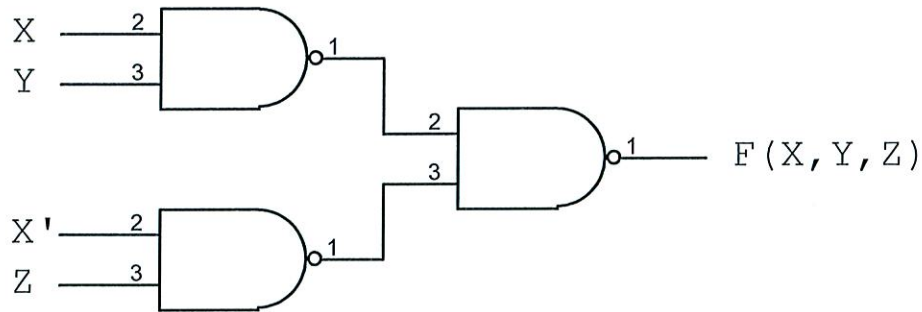Write out the function, fill out the truth table, and determine both the ON-set and the OFF-set for the function implemented by the following circuit:



$F(X,Y,Z) =$ _____

X	Y	Z	F(X,Y,Z)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

ON-set = _____

OFF-set = _____

Revisited Concept Exercise for Module 2 – No. 2

Wednesday, February 19, 2014

Compare the cost of minimal two-level NAND and two-level NOR gate implementations of the function, $F(W,X,Y,Z)$, mapped below. Show both the NAND and NOR circuit realizations and calculate the cost of each. Assume both true and complemented variables are available.

NAND realization:

NAND cost = _____

		W'		W		
Y'		0	1	1	0	Z'
		0	0	0	0	Z
Y		1	1	0	1	
		1	1	1	1	Z'
		X'	X		X'	


NOR realization:

NOR cost = _____

		W'		W		
Y'		0	1	1	0	Z'
		0	0	0	0	Z
Y		1	1	0	1	
		1	1	1	1	Z'
		X'	X	X'		

Revisited Concept Exercise for Module 2 – No. 3
Monday, February 24, 2014

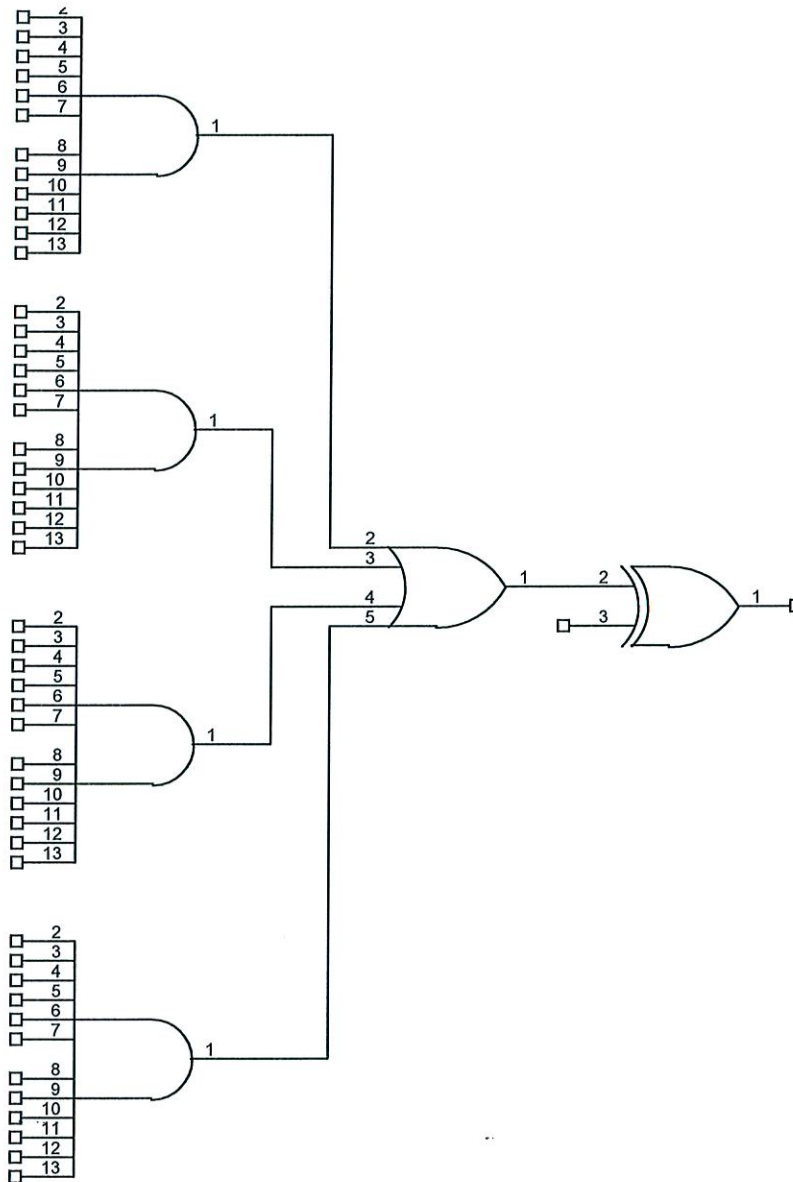Assume a hypothetical PLD has macrocells of the following configuration:



The maximum number of *product terms* that can be implemented by each macrocell = ____

The maximum number of *literals* that each product term can have = ____

Revisited Concept Exercise for Module 2 – No. 4
Wednesday, February 26, 2014

1. **A0, A1, A2, A3** defined as the set **ALL**:
2. **B0, B1, B2, B3, B4** used as a range:
3. **GE** used as the tri-state enable for output signals **G0, G1, G2, G3**:
4. Write using ABEL syntax: $G(W,X,Y,Z) = (X \oplus Z) \cdot (W \oplus Y)'$
5. Write using ABEL syntax: $F(W,X,Y,Z) = W' \cdot Z \cdot (X + Y') + Y \cdot (X' + W + Z)$
6. ABEL declaration that specifies input variables **SA, SB, and SC** are *active low*:
7. ABEL declaration that specifies variables **R0, R1, R2, and R3** are *active low* combinational outputs:
8. ABEL equation statement specifying that the *tri-state enable* for combinational output signals **R0, R1, R2, and R3** is given by the expression $A \cdot B' \cdot C$: